 


Deriving HW architectures and its control

- RTL system overview
- Deriving sequential architectures
- Strategy for complex control subsystems

RTL system design overview



Data-path

Circuitry to process the input data:

- combinational and sequential circuits

Controller

Circuitry to control the data-path operation:

- FSM

Processor: Controller and data-path components working together to implement an algorithm

Serial vs. parallel architecture

Ej: FIR filter algorithm

$$y(n) = \sum_{k=0}^{M-1} h_k x(n-k)$$





```
y(0) = 0
for k = 1 to M do
  y(k) = y(k-1) + h(k)*x(k)
end
y = y(n)
```

Operations

- Additions (+)
- Multiplications (*)
- Storage of variables (=)

Operators

    - Adder
- Multiplier
- Storage resources
(registers or memory)



Architecture derivation:

How many clock cycles do we have to obtain a result?

- N clock cycles \Rightarrow operators can be reused (several operations mapped in the same operator) \Rightarrow serial architecture
- 1 clock cycle \Rightarrow as many operators as operations \Rightarrow parallel arch.

Deriving sequential architectures

Ex. Newton-Raphson method: calculate the zeros of a function by means the following iteration:



$$\tan(\alpha_k) = f'(x_k) = \frac{f(x_k)}{x_k - x_{k+1}}$$



$$x_{k+1} = x_k - \frac{f(x_k)}{f'(x_k)}$$



$$f(x_\infty) = 0$$

  

- To choose the proper initial value x_0 is important, a wrong value can avoid the algorithm's convergence
- Quadratic convergence:
 $e_{k+1} = c \cdot e_k^2$

Deriving sequential architectures

Newton-Raphson method: reciprocal, $x=1/d$, computation

$$f(x) = 1/x - d \Rightarrow f(x) = 0 \Rightarrow x = 1/d$$

$$f'(x) = -1/x^2$$


$$x_{k+1} = x_k - \frac{f(x_k)}{f'(x_k)} \Rightarrow x_{k+1} = x_k (2 - x_k d)$$

Matlab model

```
x=x0;  
for i= 1:it  
    x=x*(2-d*x);  
end  
y=x;
```

Operations per iteration: 2 multiplications and 1 addition

Example: $d = 0.97$, $X_0 = 1.5$, ($x = 1/d = 1.030927835051547$):

1ª iteración: $X_1 = 1.5 \cdot (2 - 1.4550) = 0.8175$

2ª iteración: $X_2 = 0.8175 \cdot (2 - 0.7930) = 0.9868$

3ª iteración: $X_3 = 0.9868 \cdot (2 - 0.9572) = 1.0290$

4ª iteración: $X_4 = 1.0290 \cdot (2 - 0.9981) = 1.0309$

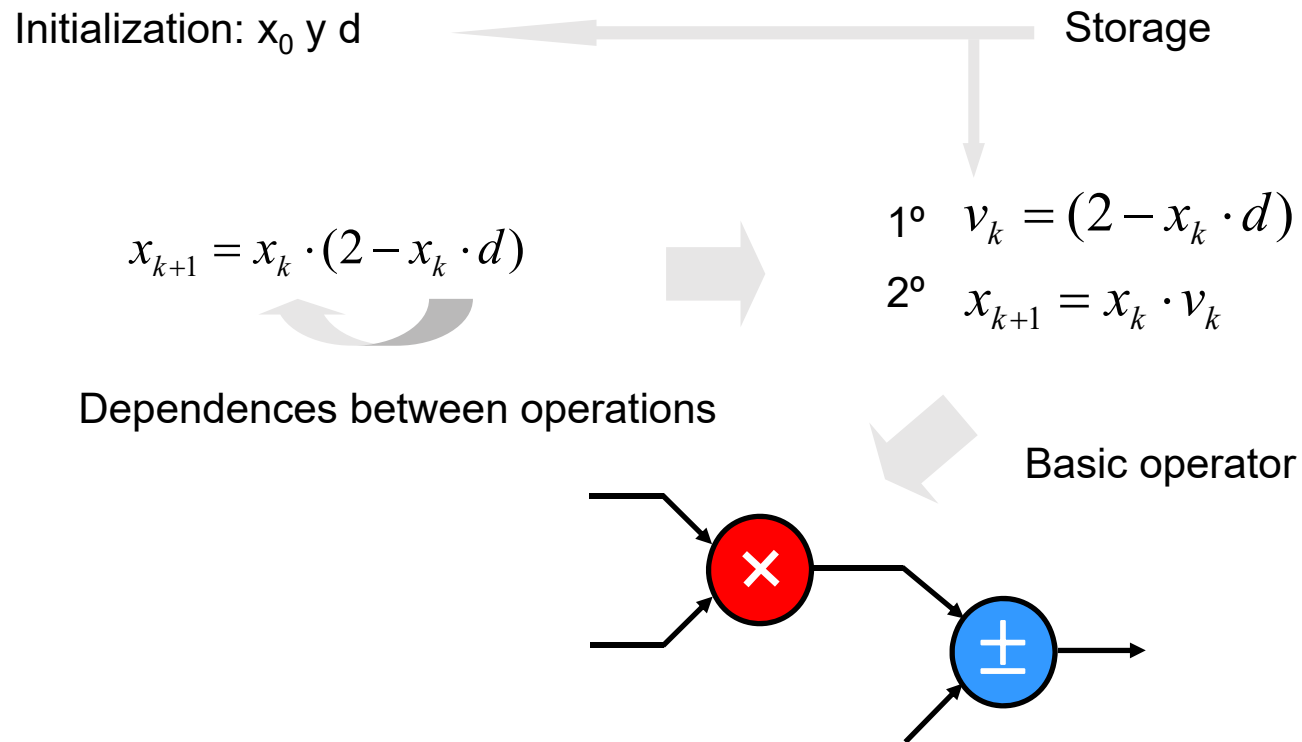

$$X_4 = 1.0309$$

$$f(X_4) = 1/x_4 - d = 1/1.0309 - 0.97 = 2.6e-5$$

Deriving sequential architectures

Newton-Raphson method: reciprocal, $x=1/d$, computation


Sequential hardware architecture with 1 multiplier



Deriving sequential architectures

Newton-Raphson method: reciprocal, $x=1/d$, computation

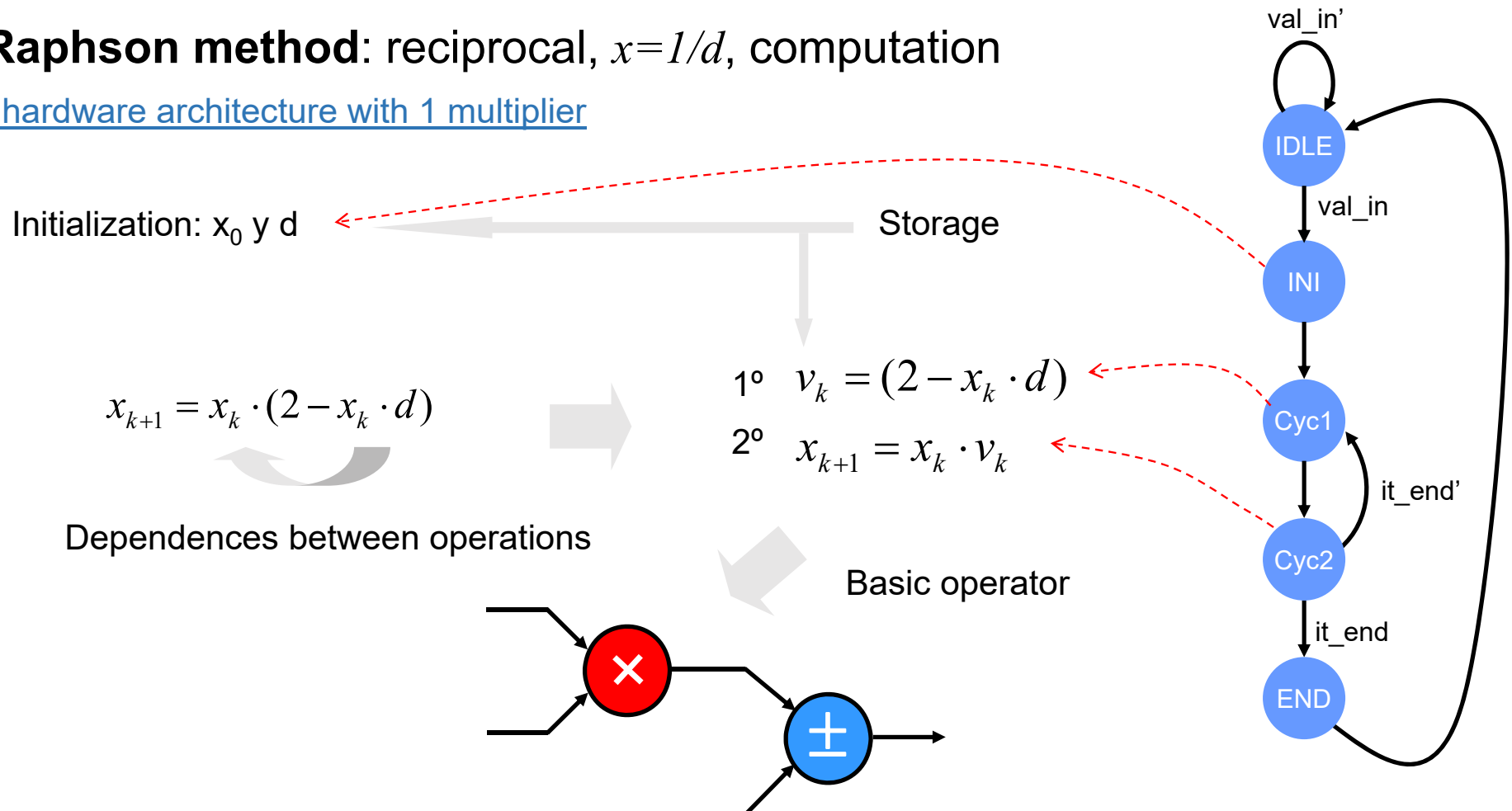Sequential hardware architecture with 1 multiplier



Deriving sequential architectures

Newton-Raphson method: reciprocal, $x=1/d$, computation

Sequential hardware architecture with 1 multiplier



Functional model

```
x=x0;  
for i= 1:it  
    x=x*(2-d*x);  
end  
y=x;
```

HW-oriented model

```
r1 = x0;  
r2 = d;  
for i = 1:it  
    % 1st cycle  
    m = r1*r2;  
    s = 2-m;  
    r_2 = s;  
    % 2nd cycle  
    m = r1*r2;  
    s = 0+m;  
    r1 = s;  
    r2 = d;  
end  
r3 = s;  
y = r3;
```

The operand's order must be kept

  

Deriving sequential architectures

Newton-Raphson method: reciprocal, $x=1/d$,

Sequential hardware architecture with 1 multiplier

HW-oriented
model



```

r1 = x0;
r2 = d;
for i = 1:it
    % 1st cycle
    m = r1*r2;
    s = 2-m;
    r2 = s;
    % 2nd cycle
    m = r1*r2;
    s = 0+m;
    r1 = s;
    r2 = d;
end
r3 = s;
y = r3;
    
```

Control sequence

```

  load_r1 = 1; sel_muxr1 = 0;
load_r2 = 1; sel_muxr2 = 0; rst_cnt=1;
for i= 1:it
    % 1st cycle
    cnt = 1;
    addsub = 1; sel_mux_as = 0;
    load_r1 = 0; load_r2 = 1; sel_muxr2 = 1;
    % 2nd cycle
    addsum = 0; sel_mux_as = 1;
    load_r1 = 1; sel_muxr1 = 1;
    load_r2 = 1; sel_muxr2 = 0;
end
load_r3 = 1;
rdy_out = 1;
    
```




Deriving sequential architectures

Newton-Raphson method: reciprocal, $x=1/d$,

Sequential hardware architecture with 1 multiplier

A good selection of x_0 improves the algorithm's convergence

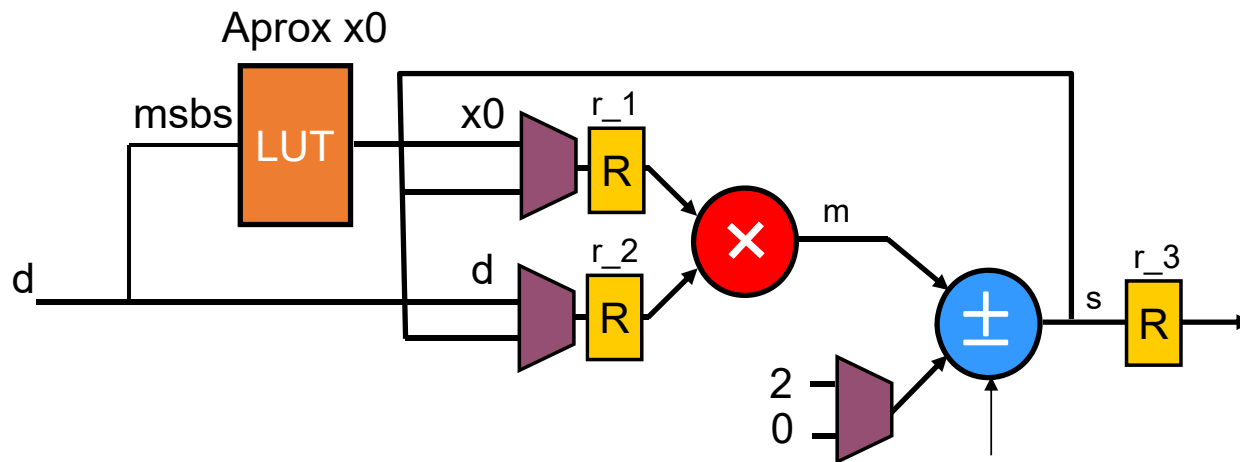⇒ a small LUT addressed by the most significant bits of d can be used




Deriving sequential architectures

Newton-Raphson method: reciprocal, $x=1/d$,

Sequential hardware architecture with 1 multiplier

Throughput?

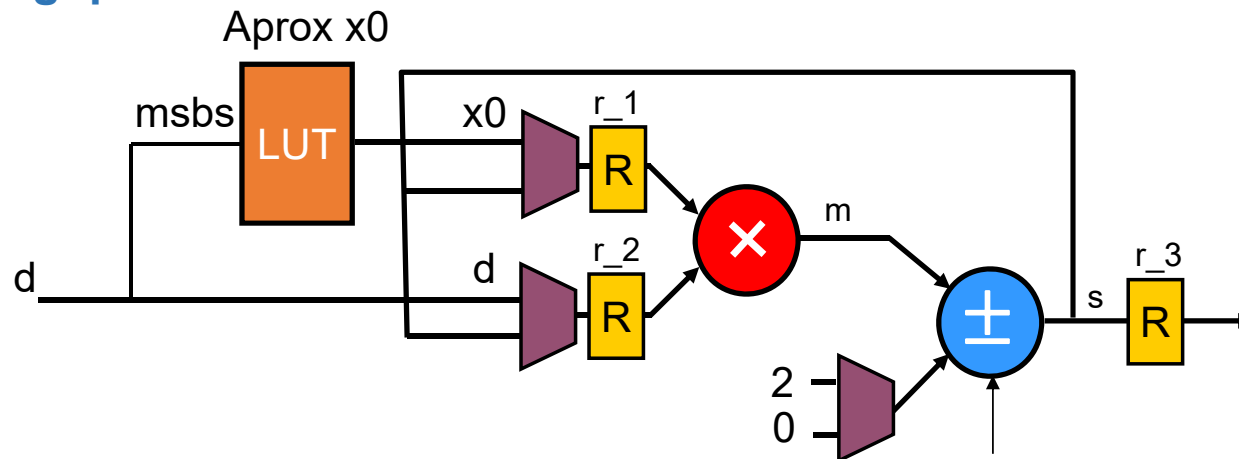

Can this architecture be pipelined to increase the throughput?

Would we increase by 2 the throughput if two multipliers were used?

Can we build a very high throughput architecture for this algorithm? How?

Modelling complex control subsystems

Complex FSMs


How to address the design of a complex control circuit?

⇒ Divide and conquer!

- Do not design a complex FSM
 - break the complex FSM down into several less-complex FSMs
- Most problems have a hierarchical solution:
 - a main FSM implements the top level of the hierarchy: ordered sequence of tasks
 - each task is developed by a specific FSM
 - the main FSM indicates when each task (FSM) must start
 - each task (FSM) alerts to the main FSM when its task is finished

Complex FSMs

⇒ **Divide and conquer!**

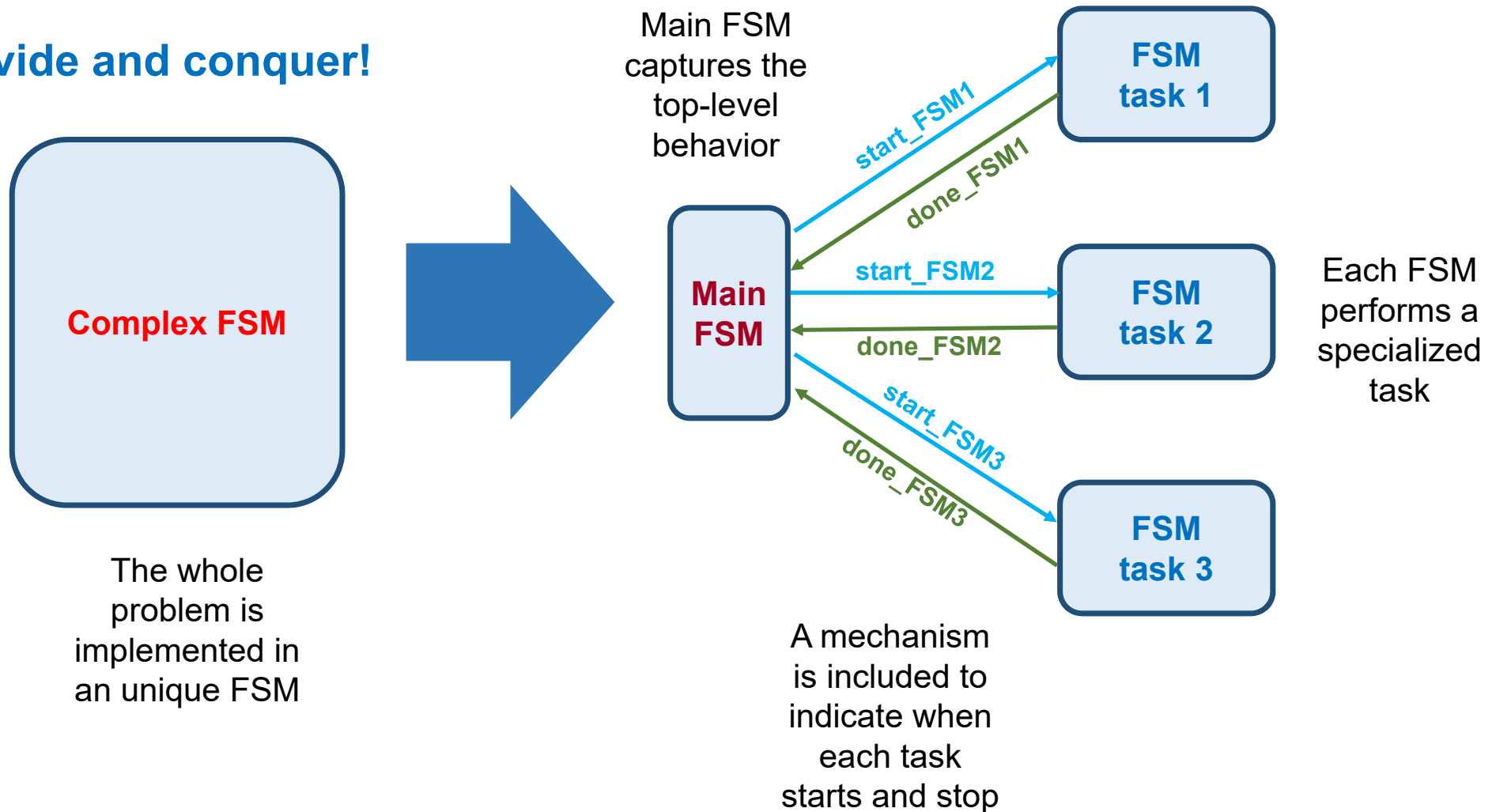

References

- S.A. Khan, Digital Design of Signal Processing Systems: A practical approach, Wiley 2011
- F. Vahid, Digital Design with RTL Design, and Verilog, Wiley 2010